

Homework #3

1.) Design a single cell - 1 bit carry propagate (Ripple Carry Adder) full adder.

(a) Generate the truth table

	INPUTS			OUTPUTS	
	A _x	B _x	C _{in}	S _x	C _{out}
r ₀	0	0	0	0	0
r ₁	0	0	1	1	0
r ₂	0	1	0	1	0
r ₃	0	1	1	0	1
r ₄	1	0	0	1	0
r ₅	1	0	1	0	1
r ₆	1	1	0	0	1
r ₇	1	1	1	1	1

(b) Using K-map, determine the logical expression for carry out (C-out) and sum (S)

$$S_x = \bar{A}_x \bar{B}_x C_{in} + \bar{A}_x B_x \bar{C}_{in} + A_x \bar{B}_x \bar{C}_{in} + A_x B_x C_{in}$$

$$S_x = A_x \oplus B_x \oplus C_{in}$$


A _x	B _x C _{in}			
	00	01	11	10
0		1		1
1	1		1	

$$C_{out} = \bar{A}_x B_x C_{in} + A_x \bar{B}_x C_{in} + A_x B_x \bar{C}_{in} + A_x B_x C_{in}$$

$$C_{out} = A_x C_{in} + A_x B_x + B_x C_{in}$$

A _x	B _x C _{in}			
	00	01	11	10
0			1	
1		1	1	1

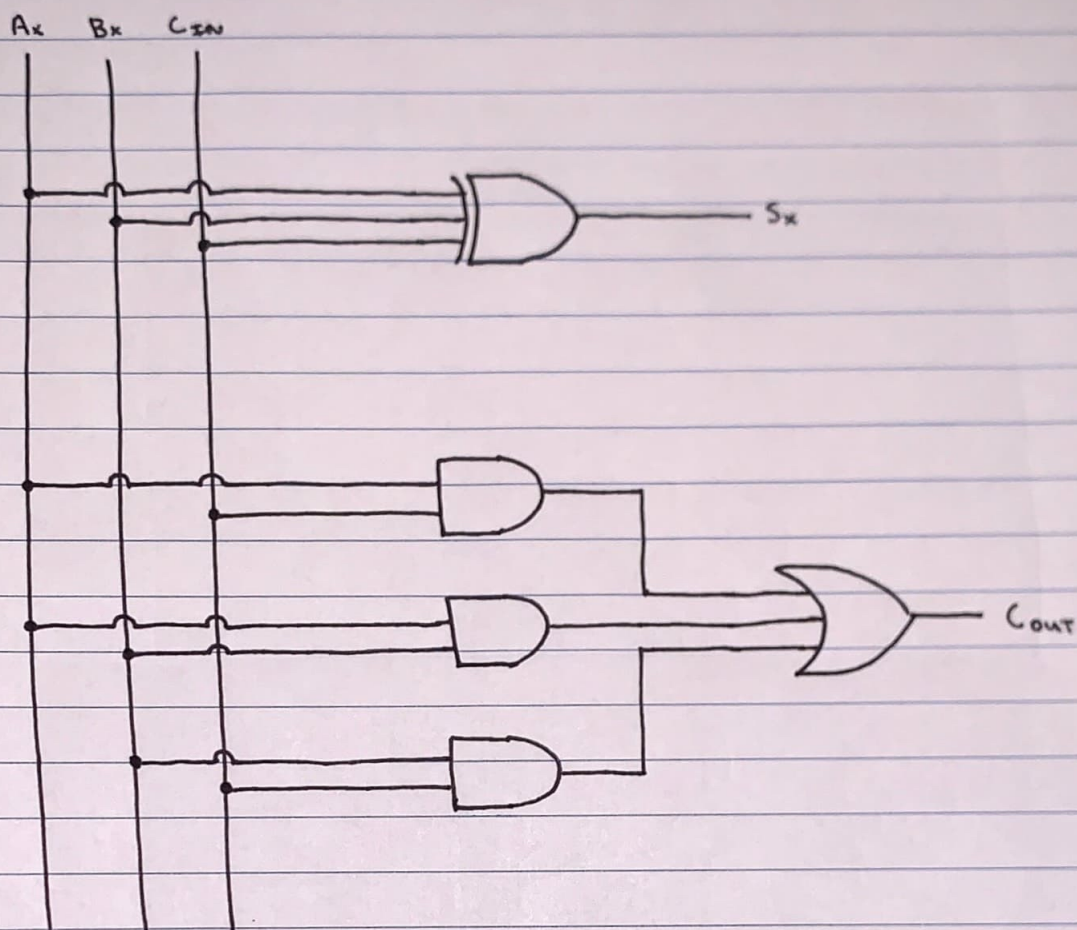© Based on the logical expression, create the schematic diagram for full adder



2.) Design a 1 bit, 2 to 1 multiplexer (Mux). Outputs Y when $S=0$; X when $S=1$.

(a) Generate the truth table

Selector	Input		Output
	X	Y	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(b) Using K-map, determine the logical expression for output

$$r = \bar{S}\bar{x}y + \bar{S}xy + S\bar{x}\bar{y} + Sx\bar{y}$$

$$r = \bar{S}y + Sx$$

s \ xy	00	01	11	10
0		1	1	
1			1	1

© Based on the logical expression, create the schematic diagram for Mux

